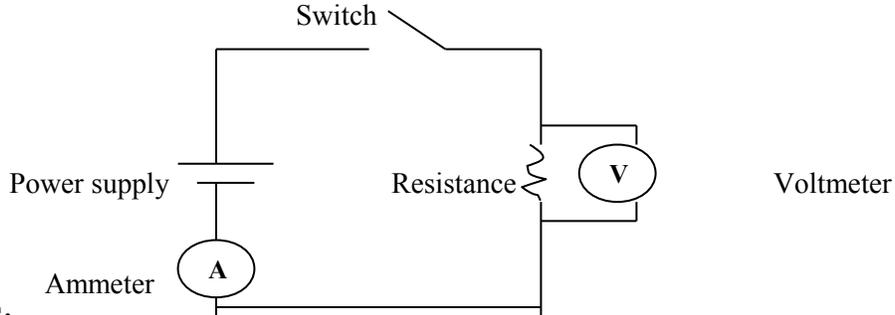


Ohm's Law

NAME _____

Ohm's Law states that if the temperature of the resistance remains constant, the electric current (I) flowing in a circuit is directly proportional to the applied voltage (V) and inversely proportional to the resistance (R) of the circuit. In other words, $I = V / R$



OBJECTIVES:

During this investigation you will determine the values of resistors by applying Ohm's law.

PROCEDURES:

- 1) Connect the source of current, the switch (opened), the ammeter, and the 2-Ω resistor (R₁) in series. Place the voltmeter in parallel across the resistance.
- 2) Make sure I have checked your circuit before you close the switch. These meters are very expensive and can easily be damaged and ruined by improper use.
- 3) Close the switch, and quickly read the meters. Open the switch as soon as the readings are completed.
- 4) Calculate the value of the resistor in ohms using Ohm's Law and enter this value in the table.
- 5) I will manually adjust the voltage to a higher reading so wait at this point until everyone has completed this step.
- 6) Once the voltage has been changed to a higher value, close the switch and once again read the meter values. Calculate the resistance, R₁ again.
- 7) I will once again adjust the voltage back to nearly the same voltage as before so hold on. Make two measurements of the resistance of the 3-Ω resistor (R₂). Repeat with a 5-Ω resistor. Enter all values in the table provided.

DATA & CALCULATIONS:

Resistor #	Printed Value of Resistor (with tolerance %) (Ω)	Voltage (V)	Current (A)	Experimental Resistance [= V / I] (Ω)	Experimental Error (%)
R ₁					
R ₁					
R ₂					
R ₂					
R ₃					
R ₃					

QUESTIONS:

- 1) Describe the proper placement of a voltmeter and an ammeter in a circuit.

- 2) Compare the printed values of your resistors with the calculated values. Be sure to mention whether or not each calculated resistance was within the tolerance range of the printed values.

- 3) If your values were not within the tolerance range of the printed values, suggest some reasons for the difference.

- 4) A 60-W light bulb has a voltage of 120 volts applied across it and current of 0.5 amperes flow through the bulb. What is the resistance of the light bulb?

EXTRA:

- 5) A piece of copper (resistivity = 1.72×10^{-6} ohm-m) 1.5 m long with a cross-sectional area of 15 cm^2 is placed across a potential difference causing a current of 4500 A. What is this potential difference?