


# Parallel Circuit Lab

NAME \_\_\_\_\_

When resistors are connected in parallel, each resistor provides a path for the electrons to follow, and therefore, reduces the total resistance to the current. In diagram below, two resistors are connected in parallel across the voltage source. There are two paths by which the current may pass from junction **a** to junction **b**. It follows that more current will flow between these junctions than would be the case if one resistor was connected between them. Each time a resistance is connected in parallel with other resistors, the total resistance decreases. The total resistance in a parallel circuit is found by:

$$1 / R_{tot} = 1 / R_1 + 1 / R_2 + \dots$$

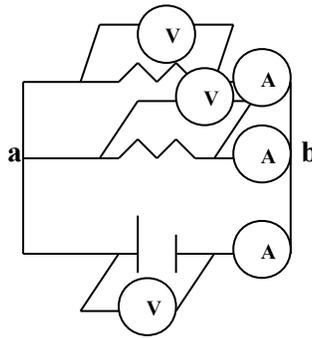Follow the circuit diagrams shown, however, **there are several meters shown and you will have only one ammeter and one voltmeter with which to obtain readings.** For example, you can take  $I_{tot}$  and  $V_{tot}$  readings, move the meters to positions  $I_1$  and  $V_1$ , and so on, until you have all the readings.



## OBJECTIVES:

During this investigation you will apply Ohm's law to a parallel circuit.

## PROCEDURES:

### Two Resistors

1) Set up the circuit as shown in the diagram, wait for me to check your set-up, plug in, and obtain your readings.

Printed value of  $R_1$  \_\_\_\_\_  $\Omega$      $R_2$  \_\_\_\_\_  $\Omega$   
 Calculated  $R_{tot}$   $[1/(1/R_1 + 1/R_2)]$  \_\_\_\_\_  $\Omega$   
 Measured  $V_1$  \_\_\_\_\_ V    Measured  $V_2$  \_\_\_\_\_ V    Measured  $V_{tot}$  \_\_\_\_\_ V  
 Measured  $I_1$  \_\_\_\_\_ A    Measured  $I_2$  \_\_\_\_\_ A    Measured  $I_{tot}$  \_\_\_\_\_ A

Measured  $R_{tot}$  (divide  $V_{tot}$  by  $I_{tot}$ ) = \_\_\_\_\_  $\Omega$   
 Measured  $I_{tot}$  (add  $I_1$  and  $I_2$ ) = \_\_\_\_\_ A  
 Measured resistance of  $R_1$  ( $V_1 / I_1$ ) = \_\_\_\_\_  $\Omega$   
 Measured resistance of  $R_2$  ( $V_2 / I_2$ ) = \_\_\_\_\_  $\Omega$

### Three Resistors

2) Set up the circuit as shown but add a third resistor in parallel with the other two. Plug in and obtain your readings.

Printed value of  $R_1$  \_\_\_\_\_  $\Omega$      $R_2$  \_\_\_\_\_  $\Omega$      $R_3$  \_\_\_\_\_  $\Omega$   
 Calculated  $R_{tot}$   $[1/(1/R_1 + 1/R_2 + 1/R_3)]$  \_\_\_\_\_  $\Omega$   
 Measured  $V_1$  \_\_\_\_\_ V    Measured  $V_2$  \_\_\_\_\_ V    Measured  $V_3$  \_\_\_\_\_ V    Measured  $V_{tot}$  \_\_\_\_\_ V  
 Measured  $I_1$  \_\_\_\_\_ A    Measured  $I_2$  \_\_\_\_\_ A    Measured  $I_3$  \_\_\_\_\_ A    Measured  $I_{tot}$  \_\_\_\_\_ A

Measured  $R_{tot}$  (divide  $V_{tot}$  by  $I_{tot}$ ) = \_\_\_\_\_  $\Omega$

Measured  $I_{tot}$  (add  $I_1$  to  $I_2$  and  $I_3$ ) = \_\_\_\_\_ A

Measured resistance of  $R_1$  ( $V_1/I_1$ ) = \_\_\_\_\_  $\Omega$

Measured resistance of  $R_2$  ( $V_2/I_2$ ) = \_\_\_\_\_  $\Omega$

Measured resistance of  $R_3$  ( $V_3/I_3$ ) = \_\_\_\_\_  $\Omega$

### INTERPRETATION & CONCLUSION:

1. Discuss specifically how your values for measured and calculated resistances compare and offer a reasonable explanation of why the values might differ.
2. Explain Kirchoff's Loop Rule and Kirchoff's Junction Rule. Which of these is simply a restatement of the Law of Conservation of Energy? Which is a restatement of the Law of Conservation of Charge?
3. What happens to the total current as additional resistors were added to your circuit? Explain this in terms of the fire hazard we see by overloading an outlet at home. What safety measures are put in place in the home to counter such hazards?